

Boolean Algebra

BME208 – Logic Circuits

Yalçın İŞLER

islerya@yahoo.com

<http://me.islerya.com>

Boolean Algebra 1/2

- A set of elements B
 - There exist at least two elements $x, y \in B$ s. t. $x \neq y$
- Binary operators: $+$ and \cdot
 - closure w.r.t. both $+$ and \cdot
 - additive identity ?
 - multiplicative identity ?
 - commutative w.r.t. both $+$ and \cdot
 - Associative w.r.t. both $+$ and \cdot
- Distributive law:
 - \cdot is distributive over $+$?
 - $+$ is distributive over \cdot ?
 - We do not have both in ordinary algebra

Boolean Algebra 2/2

- Complement
 - $\forall x \in B$, there exist an element $x' \in B \ni$
 - a. $x + x' = 1$ (multiplicative identity) and
 - b. $x \cdot x' = 0$ (additive identity)
 - Not available in ordinary algebra
- Differences btw ordinary and Boolean algebra
 - Ordinary algebra with real numbers
 - Boolean algebra with elements of set B
 - Complement
 - Distributive law
 - Do not substitute laws from one to another where they are not applicable

Two-Valued Boolean Algebra 1/3

- To define a Boolean algebra
 - The set B
 - Rules for two binary operations
 - The elements of B and rules should conform to our axioms
- Two-valued Boolean algebra
 - $B = \{0, 1\}$

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

x	x'
0	1
1	0

Two-Valued Boolean Algebra 3/3

- Two-valued Boolean algebra is actually equivalent to the binary logic defined heuristically before
 - Operations:
 - $\cdot \rightarrow$ AND
 - $+$ \rightarrow OR
 - Complement \rightarrow NOT
- Binary logic is application of Boolean algebra to the gate-type circuits
 - Two-valued Boolean algebra is developed in a formal mathematical manner
 - This formalism is necessary to develop theorems and properties of Boolean algebra

Duality Principle

- An important principle
 - every algebraic expression deducible from the axioms of Boolean algebra remains valid if the operators and identity elements are interchanged

- Example:

- $x + x = x$

- $x + x = (x+x) 1$ (identity element)
 - $= (x+x)(x+x')$ (complement)
 - $= x+xx'$ (+ over ·)
 - $= x$ (complement)

- duality principle

- $x + x = x \quad \rightarrow \quad x \cdot x = x$

Duality Principle & Theorems

- Theorem a:

- $x + 1 = 1$

- $x + 1 = 1 \cdot (x + 1)$
 $= (x + x')(x + 1)$
 $= x + x' \cdot 1$
 $= x + x'$
 $= 1$

- Theorem b: (using duality)

- $x \cdot 0 = 0$

Absorption Theorem

$$a. x + xy = x$$

$$=x.1+xy$$

$$=x(1+y)$$

$$=x$$

Involution & DeMorgan's Theorems

- Involution Theorem:
 - $(x')' = x$
 - $x + x' = 1$ and $x \cdot x' = 0$
 - Complement of x' is x
 - Complement is unique
- DeMorgan's Theorem:
 - a. $(x + y)' = x' \cdot y'$
 - b. From duality ? $(x \cdot y)' = x' + y'$

Truth Tables for DeMorgan's Theorem

$$-(x + y)' = x' \cdot y'$$

x	y	x+y	(x+y)'	x · y	(x · y)'
0	0				
0	1				
1	0				
1	1				



x'	y'	x' · y'	x' + y'
1	1		
1	0		
0	1		
0	0		

Operator Precedence

1. Parentheses

2. NOT

3. AND

4. OR

• Example:

– $(x + y)'$

– $x' \cdot y'$

– $x + x \cdot y'$


Boolean Functions

- Consists of
 - binary variables (normal or complement form)
 - the constants, 0 and 1
 - logic operation symbols, “+” and “.”
- Example:
 - $F_1(x, y, z) = x + y' z$
 - $F_2(x, y, z) = x' y' z + x' y z + xy'$

x	y	z	F ₁	F ₂
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0

Logic Circuit Diagram of F_1


$$F_1(x, y, z) = x + y' z$$

 

Gate Implementation of $F_1 = x + y' z$

Logic Circuit Diagram of F_2


$$F_2 = x' y' z + x' y z + xy'$$

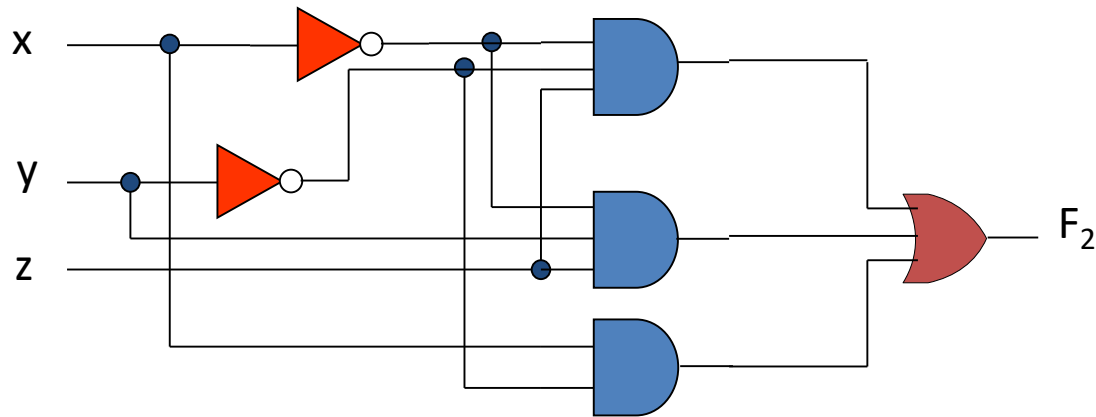


- Algebraic manipulation
- $F_2 = x' y' z + x' y z + xy'$
 $= x'z(y'+y) + xy'$

Alternative Implementation of F_2


$$F_2 = x' z + xy'$$

 


$$F_2 = x' y' z + x' y z + xy'$$

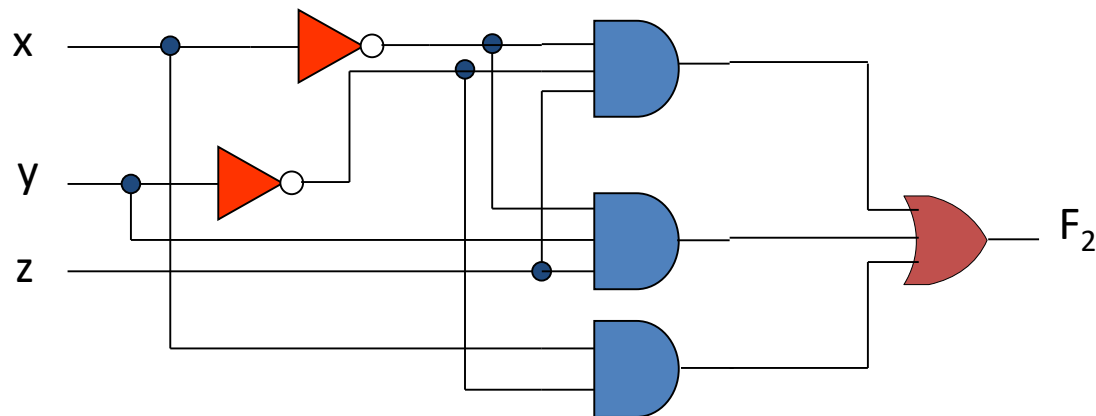


Example

 

Example

 

Example

 

$$\begin{aligned} f &= (x + y \cdot \bar{z}) \cdot \overline{(y \cdot z)} \\ &= (x + y \cdot \bar{z}) \cdot (\bar{y} + \bar{z}) \\ &= x \cdot (\bar{y} + \bar{z}) + (y \cdot \bar{z}) \cdot (\bar{y} + \bar{z}) \\ &= x \cdot \bar{y} + x \cdot \bar{z} + y \cdot \bar{z} \cdot \bar{y} + y \cdot \bar{z} \cdot \bar{z} \\ &= x \cdot \bar{y} + x \cdot \bar{z} + 0 \cdot \bar{z} + y \cdot \bar{z} \cdot \bar{z} \\ &= x \cdot \bar{y} + x \cdot \bar{z} + 0 + y \cdot \bar{z} \cdot \bar{z} \\ &= x \cdot \bar{y} + x \cdot \bar{z} + 0 + y \cdot \bar{z} \\ &= x \cdot \bar{y} + x \cdot \bar{z} + y \cdot \bar{z} \end{aligned}$$

OTHER LOGIC OPERATORS - 1

- AND, OR, NOT are logic operators
 - Boolean functions with two variables
 - three of the 16 possible two-variable Boolean functions


x	y	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

x	y	F ₈	F ₉	F ₁₀	F ₁₁	F ₁₂	F ₁₃	F ₁₄	F ₁₅
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1


OTHER LOGIC OPERATORS - 2

- Some of the Boolean functions with two variables
 - Constant functions: $F_0 = 0$ and $F_{15} = 1$
 - AND function: $F_1 = xy$
 - OR function: $F_7 = x + y$
 - XOR function:
 - $F_6 = x' y + xy' = x \oplus y$ (x or y, but not both)
 - XNOR (Equivalence) function:
 - $F_9 = xy + x' y' = (x \oplus y)'$ (x equals y)
 - NOR function:
 - $F_8 = (x + y)' = (x \downarrow y)$ (Not-OR)
 - NAND function:
 - $F_{14} = (x y)'' = (x \uparrow y)$ (Not-AND)


Logic Gate Symbols

 


NOT

 


TRANSFER

 


AND

 


XOR

 


OR

 

XNOR

 

NAND

 




NOR

Universal Gates




- NAND and NOR gates are universal
- We know any Boolean function can be written in terms of three logic operations:
 - AND, OR, NOT
- In return, NAND gate can implement these three logic gates by itself
 - So can NOR gate

x	y	$(xy)'$	x'	y'	$(x' y')'$
0	0	1	1	1	
0	1	1	1	0	
1	0	1	0	1	
1	1	0	0	0	

NAND Gate

   

NOR Gate

   


Designs with NAND gates

Example 1/2


- A function:

$$- F_1 = x' y + x y'$$

 

Example 2/2

$$- F_2 = x' y' + xy'$$

 

Multiple Input Gates

- AND and OR operations:
 - They are both commutative and associative
 - No problem with extending the number of inputs
- NAND and NOR operations:
 - they are both commutative but not associative
 - Extending the number of inputs is not obvious
- Example: NAND gates
 - $((xy)'z)' \neq (x(yz)')'$
 - $((xy)'z)' = xy + z'$
 - $(x(yz)')' = x' + yz$

Nonassociativity of NOR operation


 
 


Fig. 2-6 Demonstrating the nonassociativity of the NOR operator; $(x \downarrow y) \downarrow z \neq x \downarrow (y \downarrow z)$


Multiple Input Universal Gates

- To overcome this difficulty, we define multiple-input NAND and NOR gates in slightly different manner


Three input NAND gate: $(x y z)'$

 


Three input NOR gate: $(x + y + z)'$

 


Multiple Input Universal Gates

 

3-input NOR gate

 


3-input NAND gate

 


Cascaded NAND gates

XOR and XNOR Gates

 
- XOR and XNOR operations are both commutative and associative.
- No problem manufacturing multiple input XOR and XNOR gates
- However, they are more costly from hardware point of view.
- Therefore, we usually have 2-input XOR and XNOR gates



3-input XOR Gates

 

(a) Using 2-input gates

 

(b) 3-input gate

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(c) Truth table

Fig. 2-8 3-input exclusive-OR gate

Complement of a Function

- F' is complement of F
 - We can obtain F' , by interchanging of 0's and 1's in the truth table

x	y	z	F	F'
0	0	0	0	
0	0	1	0	
0	1	0	1	
0	1	1	0	
1	0	0	1	
1	0	1	1	
1	1	0	0	
1	1	1	0	

F =

F' =

Generalizing DeMorgan's Theorem

- We can also utilize DeMorgan's Theorem

$$- (x + y)' = x' y'$$

$$- (A + B + C)'$$

$$= (A+B)'C'$$

$$= A'B'C'$$

- We can generalize DeMorgan's Theorem

$$1. (x_1 + x_2 + \dots + x_N)' = x_1' \cdot x_2' \cdot \dots \cdot x_N'$$

$$2. (x_1 \cdot x_2 \cdot \dots \cdot x_N)' = x_1' + x_2' + \dots + x_N'$$

Example: Complement of a Function

- Example:

$$\begin{aligned} - F_1 &= x'yz' + x'y'z \\ - F_1' &= (x'yz' + x'y'z)' \\ &= (x'yz')'(x'y'z)' \\ &= (x + y' + z)(x + y + z') \\ - F_2 &= x(y'z' + yz) \\ - F_2' &= (x(y'z' + yz))' \\ &= x' + (y'z' + yz)' \\ &= x' + (y + z)(y' + z') \end{aligned}$$

- Easy Way to Complement: take the dual of the function and complement each literal

Canonical & Standard Forms

- Minterms

- A product term: all variables appear (either in its normal, x , or its complement form, x')

- How many different terms we can get with x and y ?

- $x'y' \rightarrow 00 \rightarrow m_0$

- $x'y \rightarrow 01 \rightarrow m_1$

- $xy' \rightarrow 10 \rightarrow m_2$

- $xy \rightarrow 11 \rightarrow m_3$

- m_0, m_1, m_2, m_3 (minterms or AND terms, standard product)

- n variables can be combined to form 2^n minterms

Canonical & Standard Forms

- Maxterms (OR terms, standard sums)
 - $M_0 = x + y \rightarrow 00$
 - $M_1 = x + y' \rightarrow 01$
 - $M_2 = x' + y \rightarrow 10$
 - $M_3 = x' + y' \rightarrow 11$
 - n variables can be combined to form 2^n maxterms
 - $m_0' = M_0$
 - $m_1' = M_1$
 - $m_2' = M_2$
 - $m_3' = M_3$

Example

xyz	m_i	M_i	F
000	$m_0 = x' y' z'$	$M_0 = x + y + z$	0
001	$m_1 = x' y' z$	$M_1 = x + y + z'$	1
010	$m_2 = x' y z'$	$M_2 = x + y' + z$	1
011	$m_3 = x' y z$	$M_3 = x + y' + z'$	0
100	$m_4 = x y' z'$	$M_4 = x' + y + z$	0
101	$m_5 = x y' z$	$M_5 = x' + y + z'$	0
110	$m_6 = x y z'$	$M_6 = x' + y' + z$	1
111	$m_7 = x y z$	$M_7 = x' + y' + z'$	0

$$F(x, y, z) = x' y' z + x' y z' + x y z'$$

$$F(x, y, z) = (x + y + z)(x + y' + z')(x' + y + z)(x' + y + z')(x' + y' + z')$$

Formal Expression with Minterms

xyz	m_i	M_i	F
000	$m_0 = x' y' z'$	$M_0 = x + y + z$	F(0, 0, 0)
001	$m_1 = x' y' z$	$M_1 = x + y + z'$	F(0, 0, 1)
010	$m_2 = x' y z'$	$M_2 = x + y' + z$	F(0, 1, 0)
011	$m_3 = x' y z$	$M_3 = x + y' + z'$	F(0, 1, 1)
100	$m_4 = x y' z'$	$M_4 = x' + y + z$	F(1, 0, 0)
101	$m_5 = x y' z$	$M_5 = x' + y + z'$	F(1, 0, 1)
110	$m_6 = x y z'$	$M_6 = x' + y' + z$	F(1, 1, 0)
111	$m_7 = x y z$	$M_7 = x' + y' + z'$	F(1, 1, 1)

$$F(x, y, z) = F(0,0,0)m_0 + F(0,0,1)m_1 + F(0,1,0)m_2 + F(0,1,1)m_3 + \\ F(1,0,0)m_4 + F(1,0,1)m_5 + F(1,1,0)m_6 + F(1,1,1)m_7$$

Formal Expression with Maxterms

xyz	m_i	M_i	F
000	$m_0 = x' y' z'$	$M_0 = x + y + z$	F(0, 0, 0)
001	$m_1 = x' y' z$	$M_1 = x + y + z'$	F(0, 0, 1)
010	$m_2 = x' y z'$	$M_2 = x + y' + z$	F(0, 1, 0)
011	$m_3 = x' y z$	$M_3 = x + y' + z'$	F(0, 1, 1)
100	$m_4 = x y' z'$	$M_4 = x' + y + z$	F(1, 0, 0)
101	$m_5 = x y' z$	$M_5 = x' + y + z'$	F(1, 0, 1)
110	$m_6 = x y z'$	$M_6 = x' + y' + z$	F(1, 1, 0)
111	$m_7 = x y z$	$M_7 = x' + y' + z'$	F(1, 1, 1)

$$F(x, y, z) = (F(0,0,0)+M_0) (F(0,0,1)+M_1) (F(0,1,0)+M_2) (F(0,1,0)+M_3) \\ (F(1,0,0)+M_4) (F(1,0,1)+M_5) (F(1,1,0)+M_6) (F(1,1,0)+M_7)$$

Boolean Functions in Standard Form

x	y	z	F ₁	F ₂
0	0	0	0	1
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- $F_1(x, y, z) =$

- $F_2(x, y, z) =$

Important Properties

- Any Boolean function can be expressed as a sum of minterms
- Any Boolean function can be expressed as a product of maxterms
- Example:
 - $F' = \Sigma (0, 2, 3, 5, 6)$
 $= x'y'z' + x'yz' + x'yz + xy'z + xyz'$
 - How do we find the complement of F' ?
 - $F = (x + y + z)(x + y' + z)(x + y' + z')(x' + y + z')(x' + y' + z)$
=
=

Canonical Form

- If a Boolean function is expressed as a *sum of minterms* or *product of maxterms* the function is said to be in canonical form.
- Example: $F = x + y'z \rightarrow$ canonical form?
 - No
 - But we can put it in canonical form.
 - $F = x + y'z = \Sigma (7, 6, 5, 4, 1)$
- Alternative way:
 - Obtain the truth table first and then the canonical term.

Example: Product of Maxterms

- $F = xy + x'z$

- Use the distributive law + over ·

- $F = xy + x'z$

$$= xy(z+z') + x'z(y+y')$$

$$= xyz + xyz' + x'yz + x'y'z$$

$$= \Sigma (7, 6, 3, 1)$$

$$= \Pi (4, 5, 0, 2)$$

Conversion Between Canonical Forms

- Fact:
 - The complement of a function (given in sum of minterms) can be expressed as a sum of minterms missing from the original function
- Example:
 - $F(x, y, z) = \Sigma (1, 4, 5, 6, 7)$
 - $F'(x, y, z) =$
 - Now take the complement of F' and make use of DeMorgan's theorem
 - $(F')' =$ =
 - $F = M_0 \cdot M_2 \cdot M_3 = \Pi (0, 2, 3)$

General Rule for Conversion

- Important relation:
 - $m_j' = M_j$.
 - $M_j' = m_j$.
- The rule:
 - Interchange symbols Π and Σ , and
 - list those terms missing from the original form
- Example: $F = xy + x'z$


$$- F = \Sigma(1, 3, 6, 7) \rightarrow F = \Pi(?, ?, ?, ?)$$

Standard Forms


- Fact:
 - Canonical forms are very seldom the ones with the least number of literals
- Alternative representation:
 - Standard form
 - a term may contain any number of literals
 - Two types
 1. the sum of products
 2. the product of sums
 - Examples:
 - $F_1 = y' + xy + x'yz'$
 - $F_2 = x(y' + z)(x' + y + z')$

 Example: Standard Forms

- $F_1 = y' + xy + x'yz'$
- $F_2 = x(y' + z)(x' + y + z')$



(a) Sum of Products

 

(b) Product of Sums


Fig. 2-3 Two-level implementation

Nonstandard Forms

 
- Example:

- $F_3 = AB(C+D) + C(D + E)$

- This hybrid form yields three-level implementation



 - The standard form: $F_3 = ABC + ABD + CD + CE$




Positive & Negative Logic

- In digital circuits, we have two digital signal levels:
 - H – (higher signal level; e.g. 3 ~ 5 V)
 - L - (lower signal level; e.g. 0 ~ 1 V)
- There is no logic-1 or logic-0 at the circuit level
- We can do any assignment we wish
 - For example:
 - H → logic-1
 - L → logic-0




(a) Positive logic

 


(b) Negative logic

Feedforward or Feedback

 


Feedforward or Feedback

 


$$z = x_1x_2(x_4 + x_3x_5(x_4' + y))$$

Feedforward or Feedback

 

$$z = x_1 x_2 (x_4 + x_3 x_5 (x_4' + y)) = x_1 x_2 (x_4 + x_3 x_5 x_4' + x_3 x_5 y)$$


Feedforward or Feedback

 

$$z = x_1 x_2 (x_4 + x_3 x_5 (x_4' + y)) = x_1 x_2 (x_4 + x_3 x_5 x_4' + x_3 x_5 y)$$

$$= x_1 x_2 (x_4 + x_3 x_5 + x_3 x_5 y)$$


Feedforward or Feedback

 

$$z = x_1 x_2 (x_4 + x_3 x_5 (x_4' + y)) = x_1 x_2 (x_4 + x_3 x_5 x_4' + x_3 x_5 y)$$


$$= x_1 x_2 (x_4 + x_3 x_5 + x_3 x_5 y) = x_1 x_2 (x_4 + x_3 x_5 (1 + y))$$

Feedforward or Feedback

 

$$\begin{aligned}
 z &= x_1 x_2 (x_4 + x_3 x_5 (x_4' + y)) = x_1 x_2 (x_4 + x_3 x_5 x_4' + x_3 x_5 y) \\
 &= x_1 x_2 (x_4 + x_3 x_5 + x_3 x_5 y) = x_1 x_2 (x_4 + x_3 x_5)
 \end{aligned}$$

Signal Designation - 1

 


x	y	F
L	L	L
L	H	H
H	L	H
H	H	H

- What kind of logic function does it implement?


Signal Designation - 2

x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

 

positive logic

x	y	F
1	1	1
1	0	0
0	1	0
0	0	0

 

negative logic




Another Example

x	y	F
L	L	H
L	H	H
H	L	H
H	H	L

74LS00

Integrated Circuits

   - IC – silicon semiconductor crystal (“chip”) that contains gates.
 - gates are interconnected inside to implement a “Boolean” function
 - Chip is mounted in a ceramic or plastic container
 - Inputs & outputs are connected to the external pins of the IC.
 - Many external pins (14 to hundreds)



Levels of Integration

- SSI (small-scale integration):
 - Up to 10 gates per chip
- MSI (medium-scale integration):
 - From 10 to 1,000 gates per chip
- LSI (large-scale integration):
 - thousands of gates per chip
- VLSI (very large-scale integration):
 - hundreds of thousands of gates per chip
- ULSI (ultra large-scale integration):
 - Over a million gates per chip




904 million transistors

Digital Logic Families

- Circuit Technologies
 - TTL → transistor-transistor logic
 - ECL → Emitter-coupled logic
 - fast
 - MOS → metal-oxide semiconductor
 - high density
 - CMOS → Complementary MOS
 - low power


Parameters of Logic Gates - 1

 - Fan-out
 - load that the output of a gate drives



- If a gate , say NAND, drives four such inverters, then the fan-out is equal to 4.0 standard loads.


Parameters of Logic Gates - 1

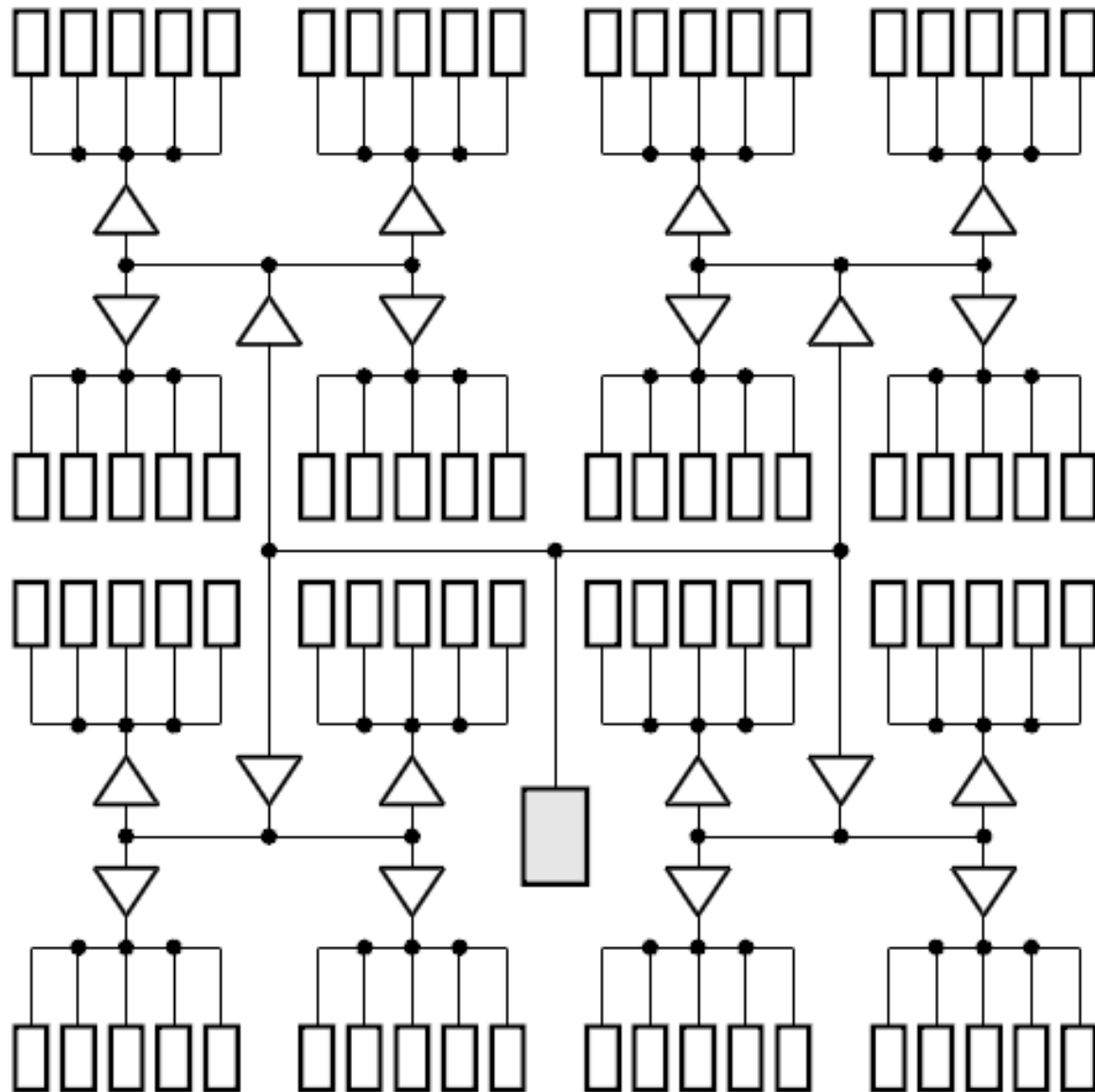

Parameters of Logic Gates - 2

- Fan-in
 - number of inputs that a gate can have in a particular logic family
 - In principle, we can design a CMOS NAND or NOR gate with a very large number of inputs
 - In practice, however, we have some limits
 - 4 for NOR gates
 - 6 for NAND gates
- Power dissipation
 - power consumed by the gate that must be available from the power supply

Power Dissipation

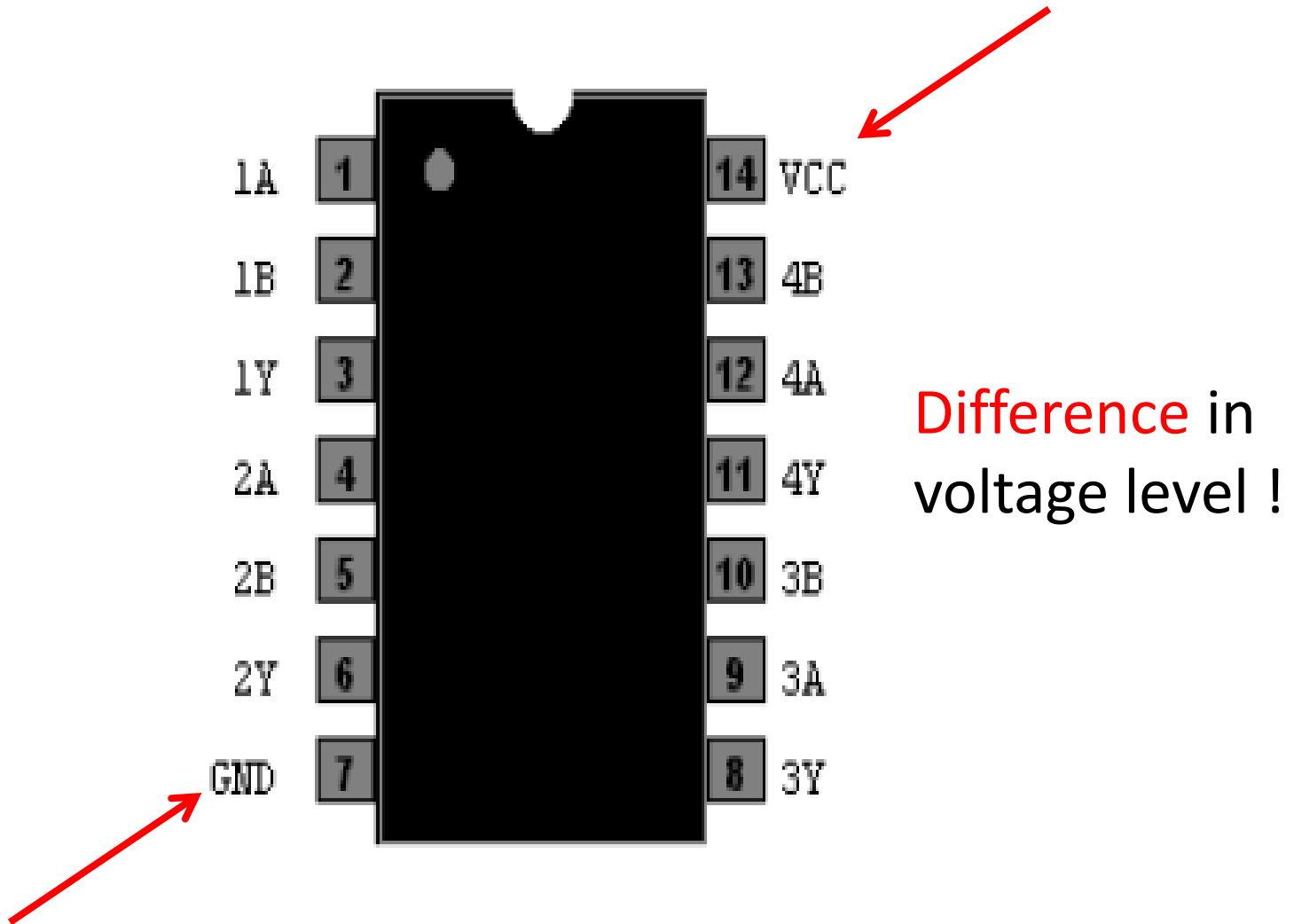

Parameters of Logic Gates - 3

- Propagation delay:
 - the time required for a change in value of a signal to propagate from input to output.

