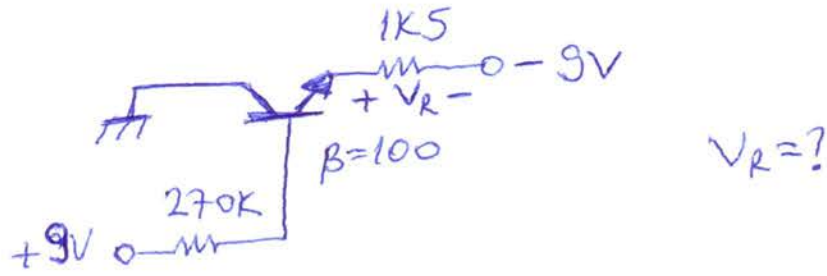


Z. K. Ü. E. E. M.
EEM301 ELEKTRONİK-1
BÜTÜNLEME SİNAVI


01.02.2012

Süre: 90 dakikadır.

10)
(28 puan)




20)
(36 puan)

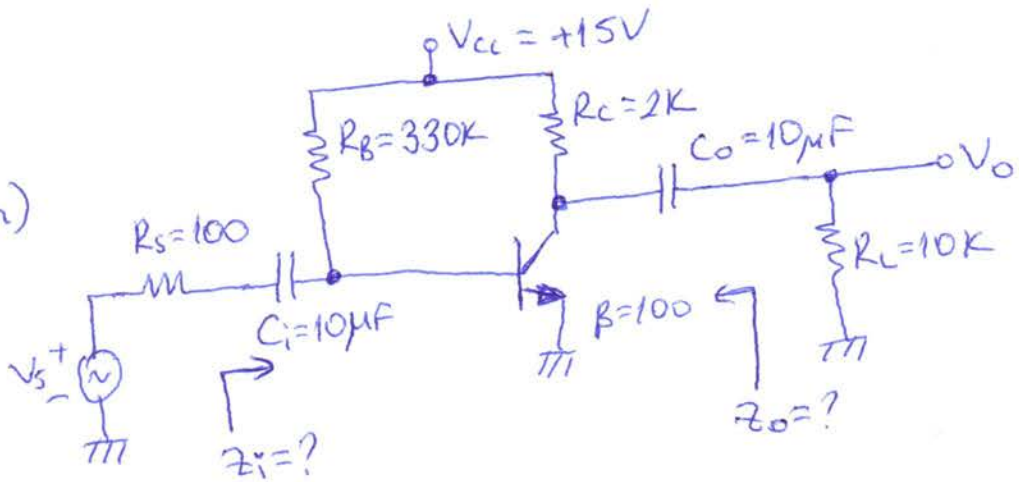


- $Z_i = ?$
- $Z_o = ?$
- $A_v = \frac{V_o}{V_s} = ?$

30)
(36 puan)

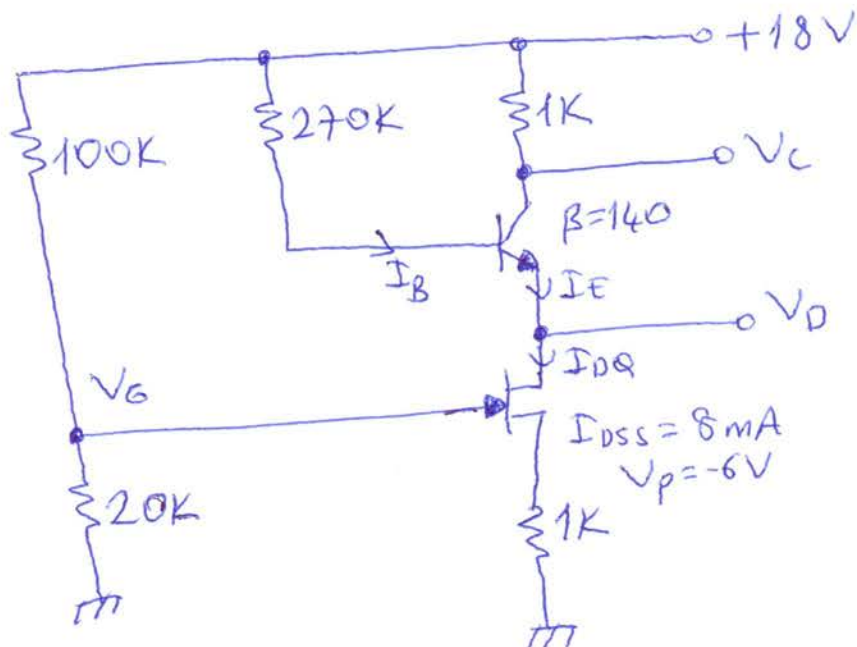

- $I_{DQ} = ?$
- $V_{CQ} = ?$
- $V_G = ?$
- $V_D = ?$
- $V_C = ?$
- $I_E = ?$

10)

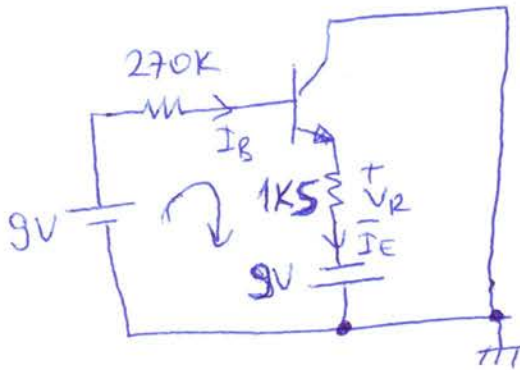

$$V_R = I_E \cdot 1K5 = (\beta + 1) \cdot I_B \cdot 1500$$

$$-9 + 270K \cdot I_B + V_{BE} + V_R - 9 = 0$$

$$270000 \cdot I_B + 1500 \cdot 101 \cdot I_B = 18 - V_{BE} = 17,3$$


$$I_B = 41 \mu A \Rightarrow V_R = 101 \cdot 1500 \cdot I_B \approx \underline{\underline{6,22 V}}$$

20) DC analizden,

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = 43 \mu A \Rightarrow I_C = 4,33 mA \text{ ve } I_E = 4,37 mA$$

$$r_e = \frac{26 mV}{I_E} = 5,95 \Omega$$

AC eşdeğerden,

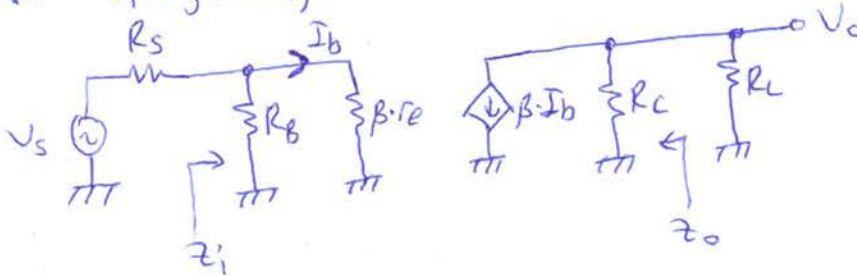

$$a) z_i = R_B // \beta r_e = 330K // 595 = \underline{\underline{593,9 \Omega}}$$

$$b) z_o = R_C = \underline{\underline{2K \Omega}}$$

$$c) V_o = -(R_C // R_L) \cdot \beta \cdot I_b$$

$$I_i = \frac{V_s}{R_s + z_i} \Rightarrow I_b = \frac{R_B}{R_B + \beta r_e} \cdot I_i$$

$$V_o = -(R_C // R_L) \cdot \beta \cdot \frac{R_B}{R_B + \beta r_e} \cdot \frac{V_s}{R_s + z_i}$$

$$A_v = \frac{V_o}{V_s} = - \frac{R_C \cdot R_L}{R_C + R_L} \cdot \frac{\beta \cdot R_B}{R_B + \beta r_e} \cdot \frac{1}{R_s + z_i} \approx \underline{\underline{-240}}$$

$$3^{\circ}) \quad V_G = \frac{18}{100K+20K} \cdot 20K = 3V \Rightarrow V_{GS} = 3 - 1K \cdot I_{DQ}$$

$$I_{DQ} = I_{DSS} \cdot \left(1 - \frac{V_{GS}}{V_p}\right)^2 = I_{DSS} \cdot \left(1 - \frac{3 - 1000 \cdot I_{DQ}}{V_p}\right)^2$$

$$\frac{I_{DQ}}{8 \cdot 10^{-3}} = 1 - 2 \cdot \frac{3 - 1000 \cdot I_{DQ}}{-6} + \left(\frac{3 - 1000 \cdot I_{DQ}}{-6}\right)^2$$

$$125 \cdot I_{DQ} = 1 + 1 - \frac{1000}{3} \cdot I_{DQ} + \frac{9 - 6000 \cdot I_{DQ} + 1000000 \cdot I_{DQ}^2}{36}$$

$$4500 \cdot I_{DQ} = 72 - 12000 \cdot I_{DQ} + 9 - 6000 \cdot I_{DQ} + 1000000 \cdot I_{DQ}^2$$

$$1000000 \cdot I_{DQ}^2 - 22500 \cdot I_{DQ} + 81 = 0$$

$$I_{D1} = 18 \text{ mA} \quad I_{D2} = 4,5 \text{ mA}$$

$$V_{GS1} = 3 - 1000 \cdot I_{D1} = -15 \text{ V}$$

$$V_{GS2} = 3 - 1000 \cdot I_{D2} = -1,5 \text{ V} \quad (\text{mantıklı})$$

$$a) \quad I_{DQ} = I_{D2} = 4,5 \text{ mA}$$

$$b) \quad V_{GSQ} = V_{GS2} = -1,5 \text{ V}$$

$$c) \quad V_G = 3 \text{ V}$$

$$f) \quad I_E = I_{DQ} = 4,5 \text{ mA}$$

$$e) \quad I_C = \frac{\beta}{\beta+1} \cdot I_E = 4,47 \text{ mA} \Rightarrow V_C = 18 - 1000 \cdot I_C = 13,53 \text{ V}$$

$$d) \quad V_D = 18 - 270000 \cdot I_B - V_{BE} = 18 - 270000 \cdot \frac{I_E}{\beta+1} - V_{BE}$$

$$V_D = 8,68 \text{ V}$$